



**B.Tech CS/BMS/EEE (Academic Session: 2023-2024)**  
**Fundamental of Electrical and Electronics (EE-101)**

**Minor Exam**

**Duration: 2 Hour**  
**Max. Marks: 40**


**Semester - I**  
**Faculty: Dr. Pinku Ranjan**

**Date: 23/09/2023**  
**Time: 10 AM -12 Noon**


**Important Instructions:**

- This is a closed book, closed notes examination.
- This question paper comprises a total of 7 questions.
- All the questions are compulsory and attempt all questions in sequence.
- All notations have their usual meanings.

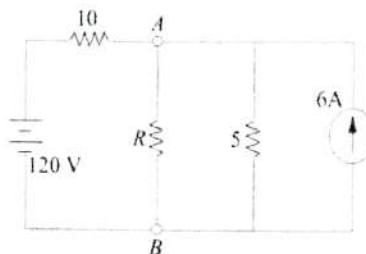
1. Calculate the value of  $R$  which will absorb maximum power from the circuit in below Fig., Also, compute the value of maximum power. **(5 Marks)**



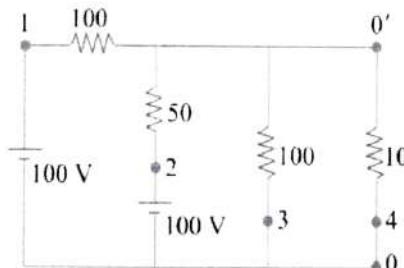
2. Calculate the voltage across the  $10\ \Omega$  resistor in the network below Fig. by using (a) Millman's theorem (b) any other method. **(10 Marks)**



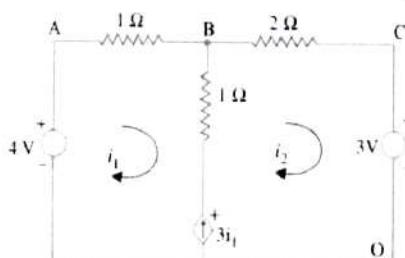
3. Find Mesh currents  $i_1$  and  $i_2$  in the electric circuit in below Fig. **(5 Marks)**



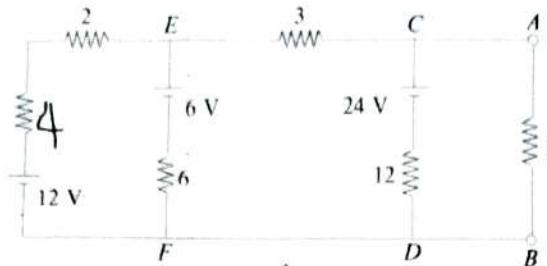
✓ 4. Using Norton's theorem, compute current through the  $1\Omega$  resistor of below Fig. (5 Marks)



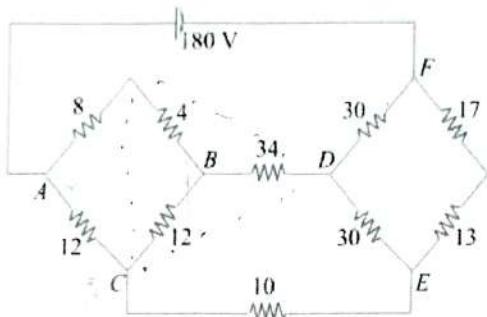✓ 5. Calculate the current flowing through the  $10\Omega$  resistor in below Fig. by using any method. (5 Marks)



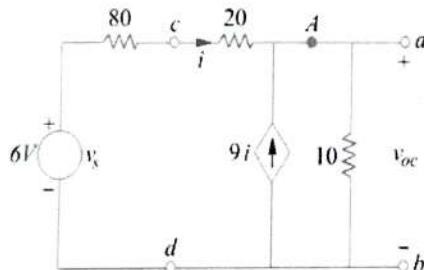6. Determine the Thevenin's equivalent circuit as viewed from the open-circuit terminals a and b of the network shown in below Fig.. All resistances are in ohms (5 Marks)



7. The resistance of the wire used for telephone is  $35\Omega$  per kilometre when the weight of the wire is  $5\text{ kg per kilometre}$ . If the specific resistance of the material is  $1.95 \times 10^{-8} \Omega\text{-m}$ , what is the cross-sectional area of the wire ? What will be the resistance of a loop to a subscriber 8 km from the exchange if wire of the same material but weighing  $20\text{ kg per kilometre}$  is used? (5 Marks)