

[No. of Printed Pages - 4]

ES103

Enrol. No. ...57.....

[ET]

END SEMESTER EXAMINATION : JANUARY, 2025

**BASIC ELECTRICAL ENGINEERING**

Time : 3 Hrs.

Maximum Marks : 60

**Note:** Attempt questions from all sections as directed. Use of scientific calculators is allowed.


**SECTION - A (24 Marks)**

Attempt any four questions out of five.

Each question carries 06 marks.



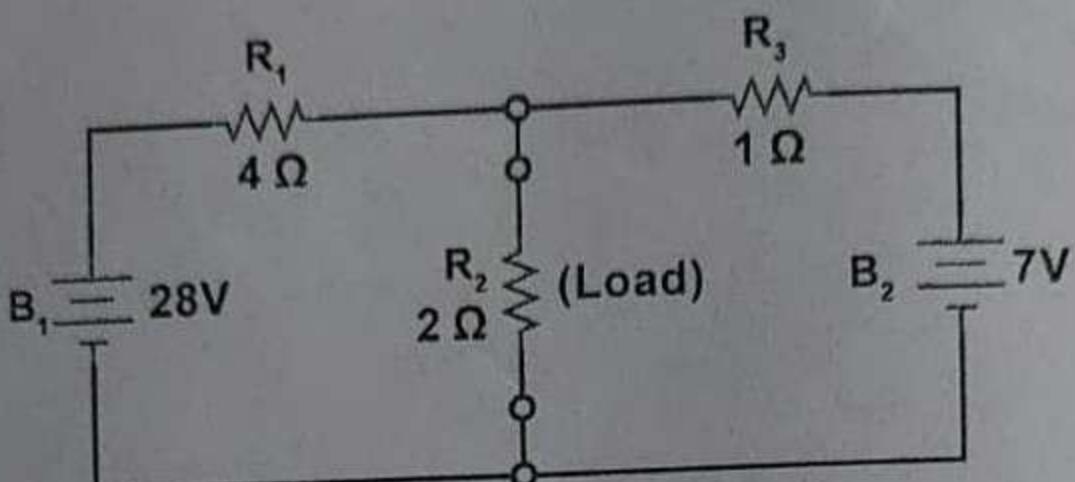State and explain Thevenin theorem. Find current in the load resistance of the circuit shown in the figure below using Thevenin theorem.



2. A single phase R-L series circuit consists of a resistance of  $20\ \Omega$  and inductance of  $0.1\ H$ . A voltage of  $240\ V$ ,  $50\ Hz$  is applied to this circuit. Find current in the circuit. Also find power consumed by the circuit and power factor of the circuit. Draw the phasor diagram.

3. Discuss the advantages, limitations and applications of PMMC and moving iron types of measuring instruments.


4. Two wattmeters connected to measure the total power in a 3-phase balanced circuit. One measures  $4800W$ , while the other reads backwards. On reversing the latter it is found to read  $400W$ . What is the total power and power factor?

5. Describe briefly the operation of a single phase transformer. Derive the expression for the induced emf of a transformer.


## SECTION - B (20 Marks)

Attempt any two questions out of three.

Each question carries 10 marks.

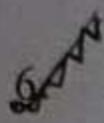

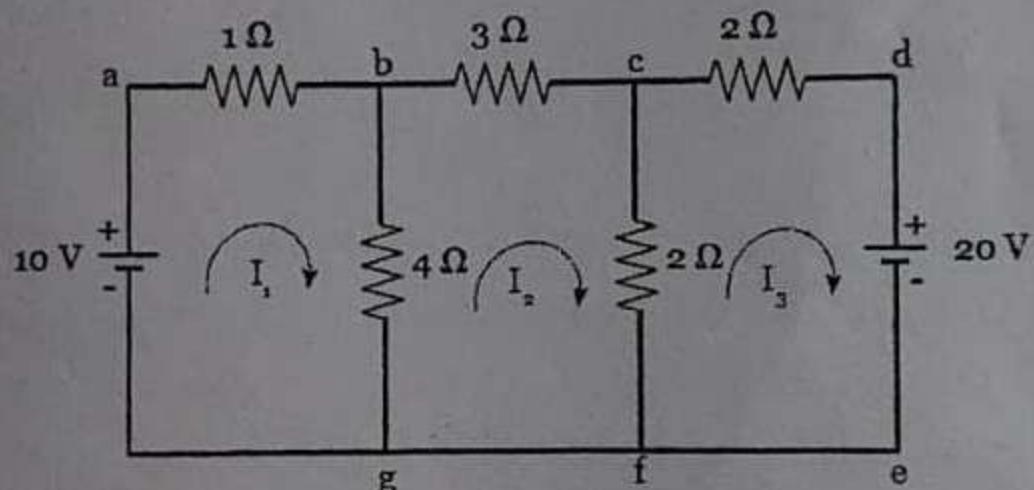State Norton's theorem for a dc network. In the circuit shown in the figure below, determine the currents  $i_1$  and  $i_2$  and  $i_3$  using mesh current method.



✓ A sinusoidally varying alternating current of frequency 60Hz has a maximum value of 15 amperes.

✓ Write down the equation for instantaneous value

(ii) ✓ Find the value of current after  $1/200$  second

(iii) ✓ Find the time taken to reach 10 amperes for the first time and

(iv) Find its average value.

6. (a) A PMMC instrument gives a reading of 25mA when the potential difference across its terminals is 75mV. Calculate shunt resistance for full scale deflection corresponding to 50A. (8)

(b) State and briefly explain Superposition theorem for a dc network. (2)

**SECTION - C (16 Marks)**

*(Compulsory)*

7. (a) Draw a circuit diagram for the measurement of power in 3 phase circuits by using two and wattmeter methods. Derive the expressions for the wattmeter readings. (8)

(b) Describe the construction and working of a transformer. A single phase transformer has a core whose cross-sectional area is 150 cm<sup>2</sup>; operates at a maximum flux density of 1.1 Wb/m<sup>2</sup> from a 50Hz supply. If the secondary winding has 66 turns, determine the output in KVA when connected to a load of 42 impedance. Neglect any voltage drop in the transformer. (8)