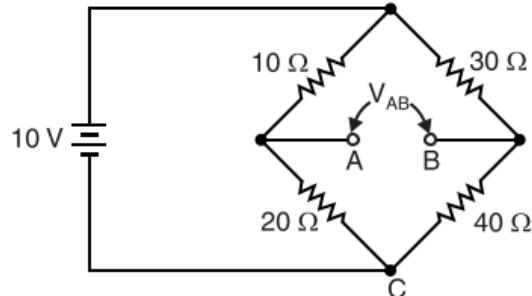
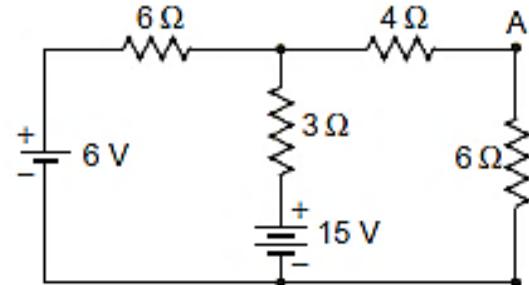



MID TERM EXAMINATION-Dec 2022(Re-minor)**Basic Electrical Engg., B. Tech-IT-1, IT-2, 1st Sem****Time: 01:00 Hrs****Maximum Marks: 30****Note: Attempt questions as per Instructions****SECTION-A (Attempt any two questions out of three, Each of 05 Marks)****Q.1.** Find the voltage V_{AB} in the circuit shown in Fig.

Q.2. State and maximum power transfer theorem and drive the condition for maximum power transfer. Also show that efficiency at maximum power transfer is 50%.

Q.3. Determine current through 6-Ω resistance connected across A–B terminals in the electric circuit shown in Figure using Thevenin's theorem.

**SECTION-B (Attempt any One question, out of two, Each of 10 Marks)**


Q.4. Use mesh current method to determine currents through each of the components in the circuit shown in Fig.

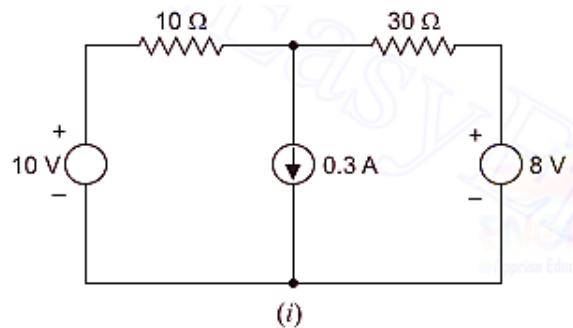**Q.5.** Discuss in brief:


- (a) Linear Circuit(s)
- (b) Mesh and Loop
- (c) Uni-lateral and Bi-lateral Network
- (d) Voltage Drop & Potential Difference
- (e) Ohm's Law

SECTION-C (Compulsory, 10 Marks)

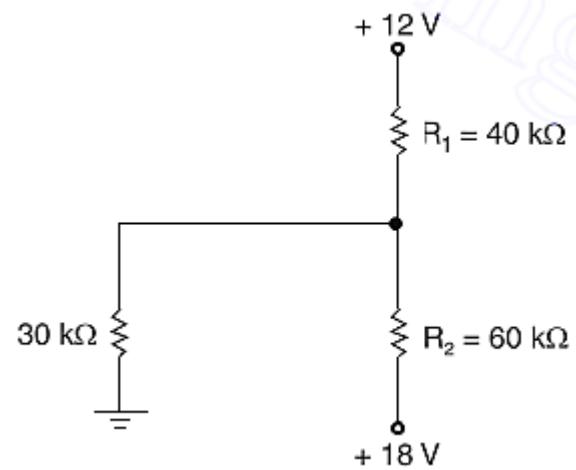Q.6. (a) Use superposition principle to find the current through resistance R_1 ($= 40 \text{ k}\Omega$) in the circuit shown in Fig. **(05Marks)**



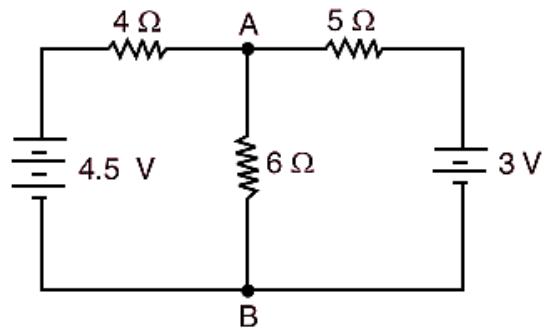(b) Using Norton's theorem, find the current in the branch AB containing 6Ω resistor of the network shown in Fig. **(05Marks)**



*****END*****