

**NATIONAL INSTITUTE OF TECHNOLOGY, KURUKSHETRA****THEORY EXAMINATION**

ROLL NO. \_\_\_\_\_

Date of the Examination: 07-05-2019

Semester...2nd

Course No.....ITPC-10

Number of Questions to be attempted...05

Total No. of Questions.....05

Programme: ....B.Tech

Subject: Digital System Design

Maximum Marks...50

Time allowed ...3 Hours

Total No. of Pages used...1

**Instructions:** 1. All questions are compulsory.

2. Marks for every part of question are indicated against it.

Q1.	(A) Express the following decimal numbers in (i) BCD code (ii) XS-3 code (iii) Gray code (iv) Hexadecimal code (v) Binary code (vi) Octal Code a) 286                      b) 807  (B) Detect and correct errors, if any, in the even parity hamming code words and write the correct code. a) 1100110    b) 0011101    c) 0111110    d) 1010111	6+4
Q2.	(A) Obtain the minimal POS expression using QM method for the following: $f = \pi M(0,1,4,5,9,11,13,15,16,17,25,27,28,29,31) \cdot d(20,21,22,30)$  (B) What is decoder? Explain BCD to seven segment decoder in detail.	5+5
Q3.	(A) What is the limitation of SR flip flop? Convert SR flip flop to JK flip flop.  (B) What is race around condition? Explain the working of master-slave JK-flip flop.	5+5
Q4.	(A) What is comparator? Explain the working of 4-bit magnitude comparator.  (B) Reduce using mapping the following expression and implement the real minimal expression in universal logic: $F = \sum m(0,2,4,6,7,8,10,12,13,15)$	5+5
Q5.	(A) What is shift register? Explain its types with the help of diagram and truth tables.  (B) Explain Johnson Counter with clock pulses.	5+5