

**NATIONAL INSTITUTE OF TECHNOLOGY, KURUKSHETRA**  
**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**  
**SESSIONAL-I**  
**CIRCUIT THEORY (ECPC-101)**

MAX. MARKS: 20

TIME: 45 MINS

1. Find the voltage drop across  $5\Omega$  resistor in the network shown in Fig. 1 using nodal analysis. 5 Marks

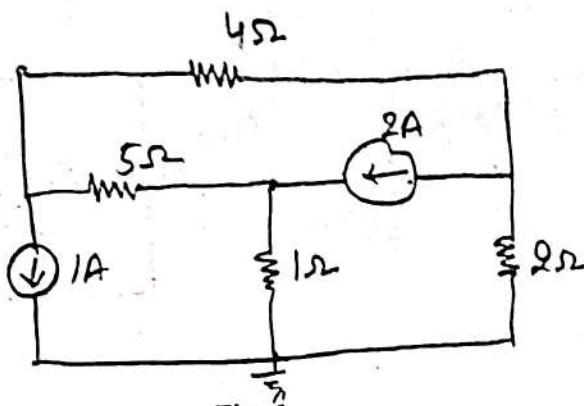


Fig. 1

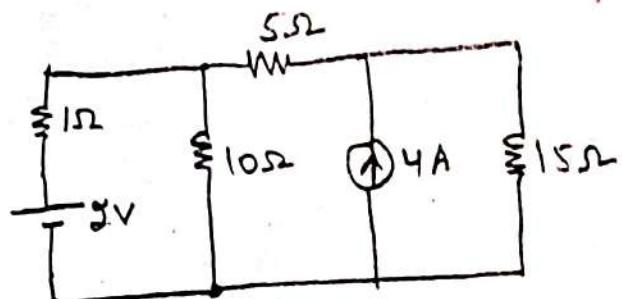


Fig. 2

2. In Fig. 2, find the current through  $10\Omega$  resistor using mesh analysis. 5 Marks

3. In Fig. 3, find  $v_x$  using superposition theorem 5 Marks

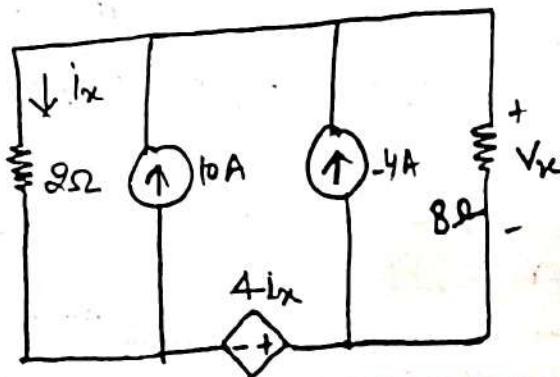


Fig. 3

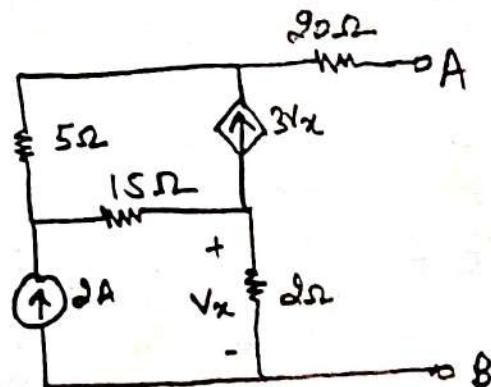


Fig. 4

4. Find the Norton's equivalent circuit across the terminals  $A-B$  in Fig. 4. 5 Marks