

Communication Engineering (ECPC-205)
Test-II (23.10.204)

Time: 50 Minutes

M.M.: 15

Q1.

- (a) Draw the circuit diagram of an AM wave generator and explain its working principle.
- (b) A transmitter radiates 19 kW power without modulation and 21.75 kW after modulation. Calculate the following (i) depth of modulation. (ii) power in USB, and (iii) power in LSB. (3+3)

Q2. Draw the circuit/block diagram of (i) a phase discriminator for generating SSB wave, (ii) Ring modulator, (iii) square law demodulator, and (iv) a narrowband FM generator. (4)

Q3.

- (a) Define frequency modulation. Derive the expression of FM signal using Bessel's function for the carrier signal $e_c(t) = A_c \cos(2\pi f_c t)$ and message signal $m(t) = A_m \cos(2\pi f_m t)$.
- (b) The frequency deviation produced on a 100 MHz carrier by a 500 Hz signal is 50 KHz. Determine the angle of phase advance and retardation produced by this signal. Also, determine the frequency deviation that would be produced by a signal of equal amplitude but of frequency 100 Hz on same carrier. (2½+2½)