

**DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING
NATIONAL INSTITUTE OF TECHNOLOGY KURUKSHETRA**

MID TEST-I

Course Name: Digital Design

Max. Marks: 20

Course Code: ECPC-202

Time Allotted: 50 Min

Date: 21.09.2024

Time: 10:30-11:20 AM

.....
Note: Q. 1 & 2 are compulsory. Solve one question from each section.

1. ~~(a)~~ Discuss different ways to detect overflow, when two signed 8-bit numbers are added (use 2's complement form). [2]
~~(b)~~ Design combinational circuits to detect overflow for above cases. [3]
2. (a) Find the minimized function for the following function: [3]
$$F(A,B,C,D) = \sum m(4,5,6,8,9,10,13) + d(0,7,15)$$

Also find the Prime Implicants (PI) and Essential Prime Implicants (EPI).
~~(b)~~ Discuss limitations of octal-to-binary encoder and how to overcome these? [2]

Section A

3. Let's design a small part of a larger design, used as part of a calendar display part of a wristwatch. You need to design a circuit to decide, based on the month of a year and whether that year is a leap year, how many days are in that month. [4]
- OR**
4. (a) Implement XOR function using only 2:1 MUXs. Draw gate level implementation. [2]
(b) Design 16:1 MUX using 2:1 MUXs only. Draw gate level implementation. [2]

Section B

5. (a) Consider 10 keypad based calculator with 0 to 9 buttons. Design a system with 7-segment based display that shows, which calculator button is pressed. [4]
(b) Design a circuit that can detect whether a pattern of at least three adjacent 1s occur anywhere in an 8-bit input. [2]
- OR**
6. (a) In a certain chemical-processing plant, a liquid chemical is used in a manufacturing process. The chemical is stored in three different tanks. A level sensor in each tank produces a HIGH voltage when the level of chemical in the tank drops below a specified point. Design a circuit that monitors the chemical level in each tank and indicates when the level in any two of the tanks drops below the specified point. Use Universal gates for the implementation. [3]
~~(b)~~ Design number-of-1s counter that count number of 1s present on 4 inputs a,b,c,d. Use universal gates. [3]