

National Institute of Technology, Kurukshetra
End Semester Exams (Theory) Dec 2022

Programme: B. Tech, ECE
Subject Code: ECPC-30
Time: Three Hours

Semester: III
Subject Name: Electronic Devices and Circuits
Max. Marks: 50

Instructions:

1. All the questions are compulsory. Internal choice as applicable
2. All parts of a question must be done at one place.
3. Unless stated otherwise, the symbols have their usual meanings in context with the subject
4. Assume suitable data, if required.

Q. No. 1 Attempt any two

2*5

- (a) Explain the difference between Zener and Avalanche breakdown.
- (b) Explain the working of FET as an amplifier with the help of a suitable diagram.
- (c) Write a short note on diffusion and transition capacitances in a diode.

Q. No. 2

2*5

- (a) Determine V_{O1} , V_{O2} , and I for the network given in Fig. 1.

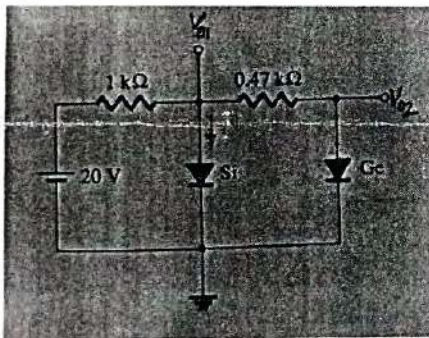


Fig. 1

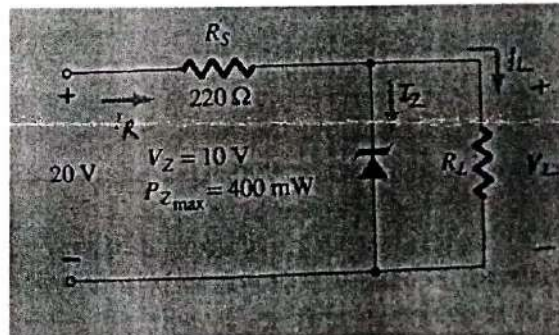


Fig. 2

- (b) Determine V_L , I_L , I_Z and I_R for the network given in Fig. 2, if $R_L = 180\Omega$. Repeat if $R_L = 470\Omega$

Q. No. 3

2*5

- (a) For the voltage divided bias configuration of Fig. 3, determine I_{BQ} , I_{CQ} , V_{CEQ} , V_C , V_E and V_B . Also, write the region of operation.
- (b) Draw the transfer and output characteristics in JFET. Define pinch off voltage and threshold voltage.

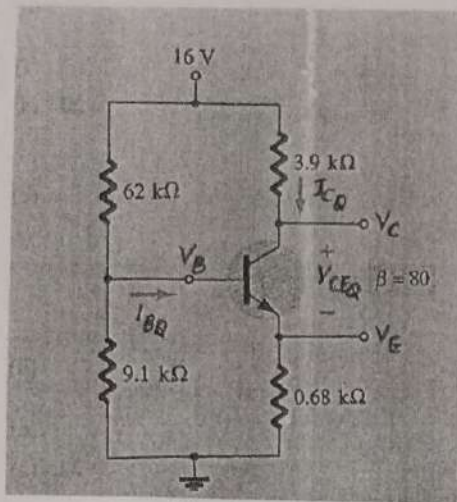


Fig. 3

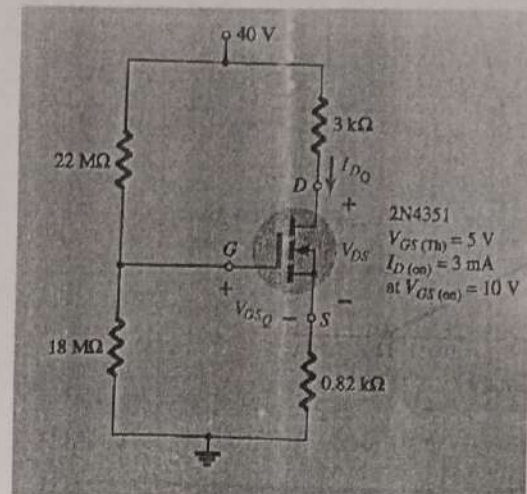


Fig. 4

Q. No. 4

2*5

- Determine I_{DQ} , V_{GSQ} and V_{DS} for the network given in Fig. 4
- Draw the r_e equivalent model for the CE configuration given in Fig. 5 and determine input impedance, output impedance, voltage gain and current gain.

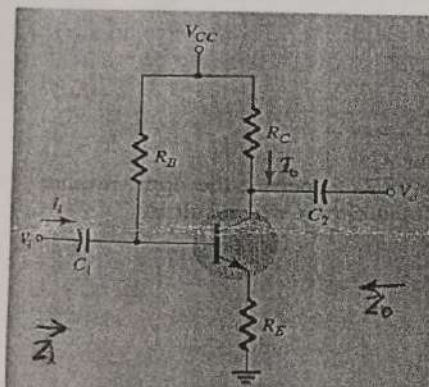


Fig. 5

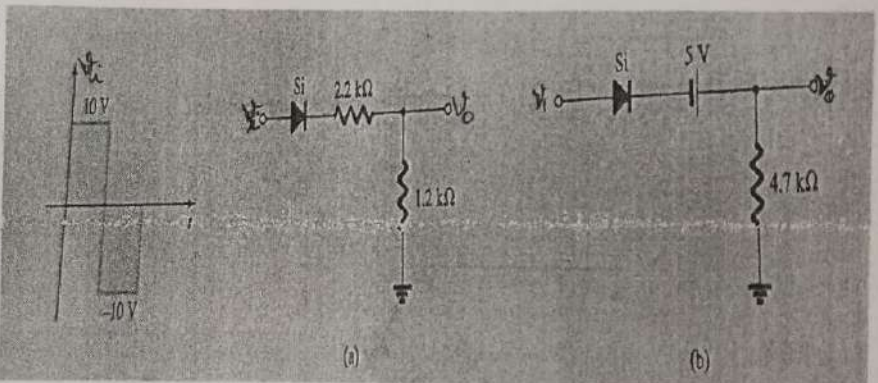


Fig. 6

Q. No. 5

2*5

- Draw the hybrid equivalent model of CE transistor and explain all the important parameters of the model.
- What is a clipper circuit? Determine v_o for each network shown in Fig. 6.