

0.0180

123105138

[ECPC-201]

NATIONAL INSTITUTE OF TECHNOLOGY KURUKSHETRA
THEORY EXAMINATION
Question Paper

Month and Year: Nov/Dec 2024
Semester 3rd
Course No.: ECPC-201
Number of questions to be attempted: 05
Total no. of questions: 05

Programme: B.Tech. (ECE)
Subject: Electronic Devices and Circuits
Maximum marks: 50
Time allowed: 3 Hrs.
No. of pages used: 02

NOTE: Attempt all questions. Assume suitable data if required.

Q.1 (a) Discuss and differentiate between Avalanche and Zener breakdown mechanism. Also draw diode equivalent circuit models. [5]

(b) Determine the currents I_1 , I_2 , and I_{D2} for the network of Fig. 1. [5]

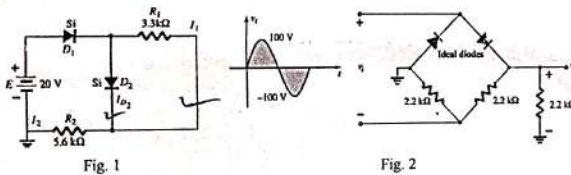


Fig. 1

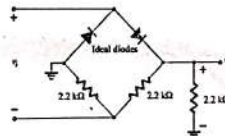


Fig. 2

Q.2 (a) Sketch V_0 for the network of Fig. 2 and determine the dc voltage available. [5]

(b) Determine V_0 for each network of Fig. 3 for the input shown. [5]

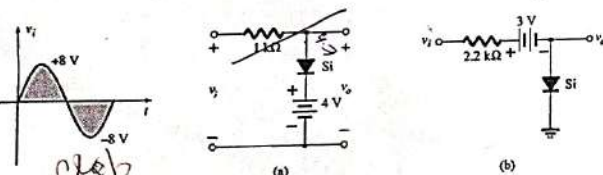


Fig. 3

[ECPC-201]

Q.3 (a) For the collector-feedback configuration of Fig. 4, determine: I_B , I_C and V_C . [5]

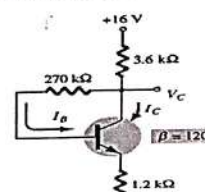


Fig. 4

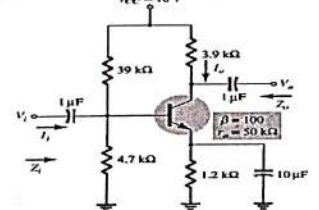


Fig. 5

(b) For the network of Fig. 5: [5]

- (i) Determine r_e (ii) Find Z_i and Z_o (with $r_o = \infty$)
- (iii) Determine A_v (with $r_o = \infty$) (iv) Repeat parts (iii) including $r_o = 25$ kΩ.

Q.4 (a) Derive the expression of input impedance, output impedance, voltage gain and current gain of Common-Emitter configuration using complete hybrid model. [5]

(b) Explain the working of n-channel MOSFET stating depletion, weak and strong inversion conditions. Also draw the I-V characteristics. [5]

Q.5 (a) Derive the expression of input impedance output impedance, voltage gain of common-source MOSFET configuration. [5]

OR

(b) Explain the working of phase shift oscillator and derive the expression of frequency.

(c) Briefly explain the working of n-channel JFET. Also describe the following terms in connection to the MOSFET: [5]

- i. Channel length modulation
- ii. Drain Induced Barrier Lowering

$$0.7 - I_1 R_1 = 0 \Rightarrow 20 - 0.7 - 0.7 - 1(5.6k) = 0$$