

MID TERM EXAMINATION - November 2024

lom h	Semester	:	Interim Semester 2024-25
Programme : B.Tech.	Course Code	:	EEE1001
mid blocker the tracks	Slot	:	B21+B22+B23
Date/Session: 6 Nov 2024/Session	Max. Marks	:	50
Time : 1 ½ hours			

Answer all the Questions

Sub


Q.No. .

Question Description


Marks

Sec.

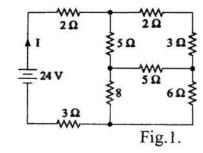1 (a) Calculate the total current supplied by the battery shown in Fig.1.



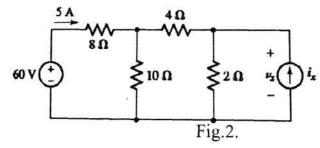1 (b) Determine v_x in the given circuit shown in Fig.2.



2 (a) Determine the current through the load resistance connected across the terminals A and B using mesh analysis shown in Fig.3.

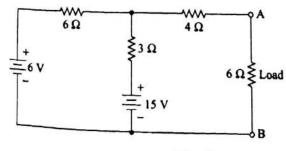


Fig.3.

2 (b) State Superposition theorem.

Calculate the value of load resistance R_L for which maximum power transfer will occur from source to load. Also calculate the value of maximum power in the given circuit shown in Fig.4.

6

2

8

2

8

5

5

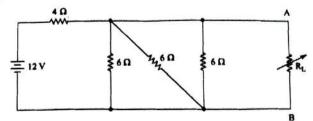


Fig.4.

- 3 (a) Show that current in a pure inductive circuit lags the voltage by 90°.
- What should be the value of R for which a current of 25 A will flow through it in the given circuit shown in Fig.5.

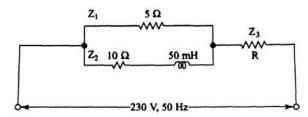


Fig.5

- 4 (a) An R-L-C series circuit has $R = 10 \Omega$, L = 0.1 H, and $C = 8 \mu F$. Calculate the resonant frequency.
- 4 (b) Consider a linear time inverse system given by

$$\frac{d^{2}y(t)}{dt^{2}} - 9\frac{dy(t)}{dt} + 14y(t) = \frac{dx(t)}{dt} + 2x(t)$$
$$x(t) = e^{-2t} u(t)$$

Find natural response, forced response, and total response for initial condition: y(0) = 5, $\frac{dy(0)}{dt} = 0$.

- 5 (a) A circular coil of radius r metres is carrying a current of I Amperes. Determine the magnetic field strength H at a point P which is situated at a distance of d metres from the centre of the coil. Also, determine the field strength at the centre of the coil.
 - (b) An iron ring with permeability 2000 has a mean length of an iron path of 1 m and has a uniform cross-sectional area of 10 cm². It is wound with two magnetizing coils in a manner such that the current flowing through the two coils produce flux in opposite directions. A cut in the ring creates an air gap of 0.1 cm. Calculate the flux.