

Reg. No.:

Name :



**VIT<sup>®</sup>**  
**BHOPAL**  
www.vitbhopal.ac.in

**Mid-Term Examinations – October 2021**

Programme	: <b>B. Tech.</b>	Semester	: <b>Fall 2021-22</b>
Course	: <b>Electric Circuits &amp; Systems</b>	Code	: <b>EEE1001</b>
Faculty	: <b>Mr. Amit Kumar Singh</b>	Slot/ Class No.	: <b>A11+A12+A13/0600</b>
Time	: <b>1 ½ hours</b>	Max. Marks	: <b>50</b>

**Answer all the Questions**

Q.No.	Sub. Sec.	Question Description	Marks
1	(a)	Derive the condition for the maximum power transfer in a given circuit.	4
	(b)	Determine the value of $R_L$ for the maximum power transfer as shown in Figure 1, also find the maximum power transferred to the load.	

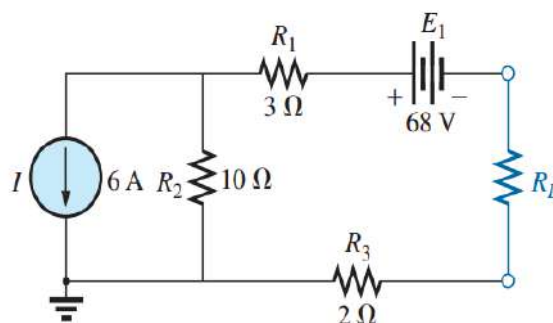


Figure 1

- 2 (a) A series  $RLC$  circuit with  $L = 160$  mH,  $C = 100$   $\mu$ F, and  $R = 40.0\Omega$  is connected to a sinusoidal voltage  $V(t) = 40\sin\omega t$ , with  $\omega = 200$  rad/s.
1. What is the impedance of the circuit?
  2. Let the current at any instant in the circuit be  $I(t) = I_0 \sin(\omega t - \phi)$ . Find  $I_0$ .
  3. What is the power factor?
- (b) Using superposition theorem, determine the current  $I_2$  through  $R_2 = 12$  K $\Omega$  resistor for the circuit shown in Figure 2.

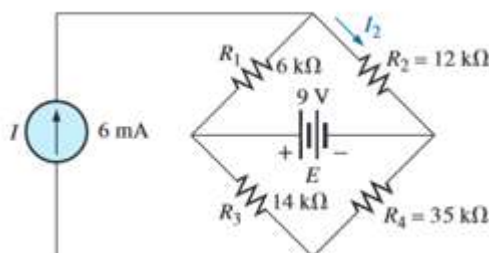


Figure 2

- 3 (a) Determine the value of " $V_o$  &  $I$ " in the circuit shown in Figure 3 considering the diodes approximate ideal.

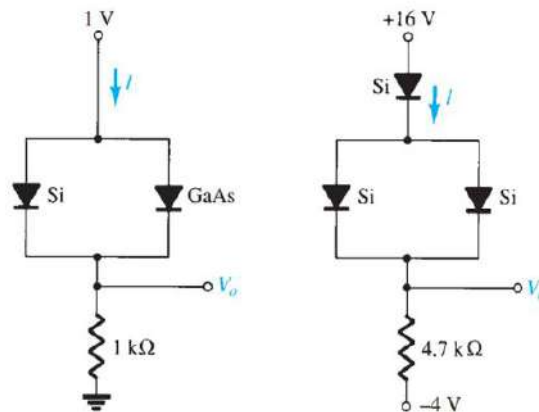


Figure 3

- (b) Determine the output waveform ( $V_o$ ) in the network shown in Figure 4 and calculate the output D.C level and required PIV of each diode?

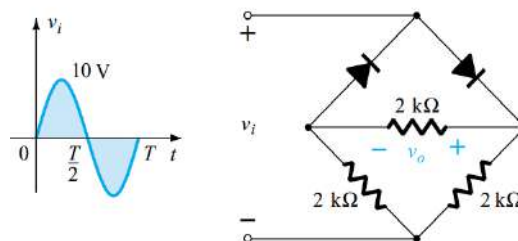


Figure 4

- 4 (a) Draw the input/ output characteristics of the CE configuration NPN transistor made up with silicon. Also define the term  $I_{CEO}$
- (b) Explain the working of n-channel D-MOSFET with the transfer characteristics curve
- 5 (a) Design a combinational logic circuit with 3 input variables that will produce logic '1' output when more than one input variables are at logic '0'.
- (b) Minimize the following Boolean function using K-map and realize it using NAND gates only

$$F(A, B, C, D) = \sum (0, 2, 5, 7, 11, 14)$$

⇔⇔⇔