



**Mid-Term Examinations - Sept. 2023**

Programme	: B.Tech – BEC, BAC, BSA	Semester	: Fall 2023-24
Course/Code	: Digital Logic Design/ ECE2002	Slot	: B11+B12+B13+B14
Time	: 1½ hours	Max. Marks	: 50

**Answer all the Questions**

- | Q. No. | Question Description  | Marks |
|--------|---|-------|
| 1      | <p>a. Determine the results for the following number conversions.</p> <p>i. Convert decimal 27.315 to binary.</p> <p>ii. Calculate the binary equivalent of <math>2/3</math> out to eight places. Then convert from binary to decimal. How close is the result to <math>2/3</math>?</p> <p>b. Determine the base of the numbers in each case for the following operations to be correct:</p> <p>(i) <math>23 + 25 = 51</math> (ii) <math>\frac{52}{2} = 12</math></p> | 6+4   |
| 2      | <p>Determine the solution of following using complement form:</p> <p>a. Add <math>-31.5_{10}</math> to <math>-93.125_{10}</math> using 12-bit 2's complement form.</p> <p>b. Subtract <math>27.50_{10}</math> from <math>68.75_{10}</math> using the 12-bit 1's complement form.</p> <p>c. Subtract <math>-25_{10}</math> to <math>+14_{10}</math> using 5-bit 2's complement form and also verify your answer. Justify the reason, if the answer is incorrect.</p>   | 3+3+4 |
| 3      | <p>Given the Boolean function</p> $F(W, X, Y, Z) = \sum m(0, 1, 4, 6, 7, 8, 10, 14, 15)$ <p>a. Determine and write down the number of implicants, prime implicants (PI) and essential prime implicants (EPI).</p> <p>b. Using K-Map find the reduced Boolean expression of the <math>F(W, X, Y, Z)</math> with minimum literals.</p> <p>c. Realize the final output using NAND or NOR logic, separately.</p>  | 3+3+4 |
| 4      | <p>Design a combinational circuit with input variables, <math>A, B</math> and <math>C</math>, and three output variables, <math>x, y</math>, and <math>z</math>.</p> <p>When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input.</p> <p>When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.</p>   | 10    |
| 5      | <p>Implement the following Boolean function with a 8:1 multiplexer:</p> <p>(a) <math>F(A, B, C, D) = \sum m(0, 2, 5, 8, 10, 14)</math></p> <p>(b) <math>F(A, B, C, D) = \sum m(2, 6, 11)</math></p>   | 10    |

⇔⇔⇔