

J.C. Bose University of Science and technology, YMCA, Faridabad
B. Tech 1st semester Mechanical Engineering
Sessional 2nd (Electrical Technology (ESC-101))

Max. Time 90 minutes

Max. Marks 15

Note. Attempt any three questions.

- | | | |
|-----|--|---|
| Q1. | A resistance of $20\ \Omega$ and a coil of inductance $31.8\ \text{mH}$ and negligible resistance are connected in parallel across $230\ \text{V}$, $50\ \text{Hz}$ supply. Find (i) the line current (ii) power factor and power consumed by the circuit | 5 |
| Q2. | What is series resonance? Derive the expression for resonant frequency in R-L-C series circuit. | 5 |
| Q3. | Draw and explain the two wattmeter method of power measurement in a three phase circuit. | 5 |
| Q4. | Derive emf equation for single phase transformer. Draw phasor diagram of single phase transformer for inductive and capacitive load. | 5 |
| Q5. | Explain working of auto transformer. What are the advantages of auto transformer over two winding transformer? | 5 |