

## Department of Mechanical Engineering

Sessional I<sup>st</sup> (Mechanical Engg. and Robotics & AI Engg. 1<sup>st</sup> Semester)

Basic Electrical Technology (ESC101A)

Time: 1:30 hrs

M. Marks: 15

Note: Part – Attempt any three questions.

Q.1) By using mesh analysis, determine the current supplied by each battery in the given circuit. (CO1) (5)

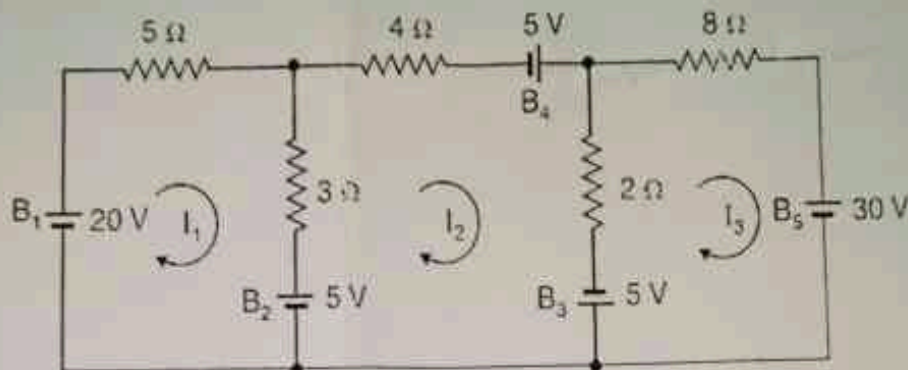


Fig-1

Q.2) State and explain maximum power transfer theorem. Derive the condition for maximum power transfer. State the applications of maximum power transfer theorem. (CO1) (5)

Q.3) Determine voltage across the 4Ω resistor using superposition theorem, in the circuit shown in Fig.2 (CO1) (5)

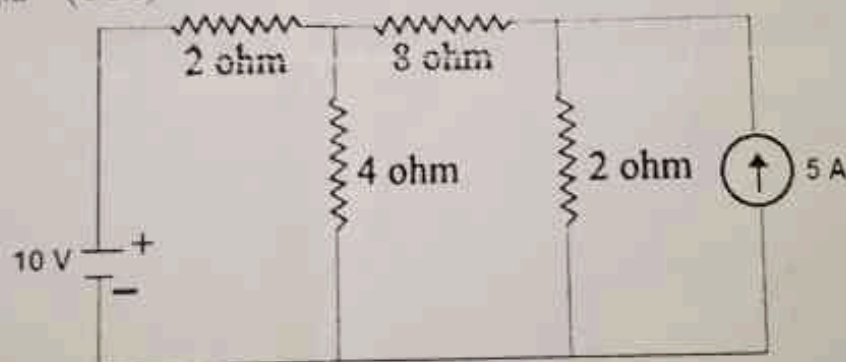


Fig-2

Q.4) Determine the current flowing in 4 ohm resistance using Thevenin's theorem in the network shown in fig.3 (CO1) (5)

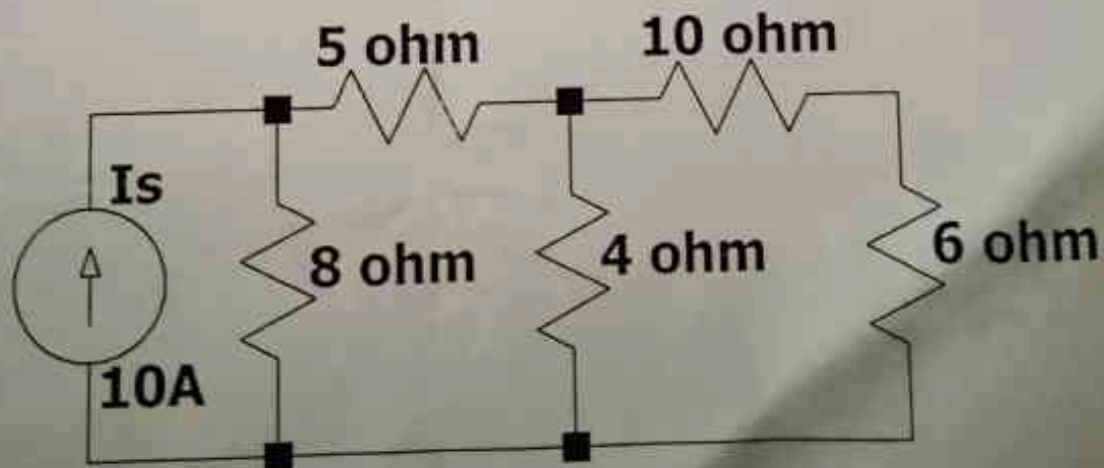


Fig-3