

J. C. Bose University of Science & Technology, YMCA Faridabad

Department of Electrical Engineering

Sessional 2nd (B. Tech 1st Sem R&AI) M112 M12

Basic Electrical Technology (ESC101A)

Session July 2025-Dec 2025

Time: 1:30 Hrs

M. Marks: 15

Note: It is compulsory to answer all the questions of Part -A in short. Attempt any two questions from part-B.

PART-A

- Q.1.a) Define the term power factor. (CO2) (1)
- b) Add voltage $V_1 = (-8 + j 6)$ volts to $V_2 = (10 + j 5)$ volts and express the result in polar form. (CO2) (1)
- c) Why transformer cores are laminated? (CO3) (1)
- d) Write any three advantages of three-phase system over single-phase system. (CO2) (1)
- e) What is the function of commutator in a DC machine? (CO3) (1)

PART-B

- Q.1) A resistance of 20Ω is connected in series with a capacitance of $100 \mu\text{F}$ across a 250V, 50 Hz supply. Find circuit impedance, current supplied, active power, and power factor. Draw a neat phasor diagram also. (CO2) (5)
- Q.2) Three identical inductive loads of resistance 20Ω and reactance 15Ω per phase are connected in star to a 400 V, 3-phase supply. Calculate (i) phase current (ii) line current and (iii) active and reactive power. (CO2) (5)
- Q.3) Explain the working of a single-phase transformer at no load condition. Draw the phasor diagram and equivalent circuit at no load. (CO3) (5)
- Q.4) Describe construction and working of three phase induction motor. (CO3) (5)