

Roll No. 23001003083

Total Pages : 03

011303

December 2024

B. Tech. (Third Semester)

Digital Electronics (ESC-302)

Time : 3 Hours]

[Maximum Marks : 75

**Note :** It is compulsory to answer all the questions (1.5 marks each) of Part A in short. Answer any *four* questions from Part B in detail. Different sub-parts of a question are to be attempted adjacent to each other.

**Part A**

1. (a) Implement the NAND gate using the NOR gate only. 1.5
- (b) Define volatile and Non-volatile memory. 1.5
- (c) Simplify the expression using Boolean algebra : 1.5  
$$Y(A, B, C) = ABC + A\bar{B} + AB\bar{C}$$
- (d) Draw block diagram of PLA. 1.5
- (e) What are the advantages of CMOS logic families used for implementing logic gates ? 1.5

- (f) Differentiate between JK and SR flip-flop. 1.5
- (g) Enlist significant specifications of ADCs. 1.5
- (h) What do you mean by quantization for A/D converters ? 1.5
- (i) What is synchronous counter ? 1.5
- (j) What is a De-multiplexer ? 1.5

### Part B

2. (a) Minimize the following function using K-map. 10  

$$F(A, B, C, D) = \sum m (0, 1, 3, 4, 7, 8, 9, 11, 14, 15)$$
- (b) An 8-bit successive approximation ADC is driven by a 1MHz clock. Find the conversion time. 5
3. (a) Convert the RS flip-flop to T-flip-flop. 5
- (b) Design BCD-counter using flip-flop. 10
4. (i) What are the error detection and correction codes ?
- (ii) Simplify the Boolean expression using D' Morgan's law

$$Y(A, B) = (\overline{A + B}) (\overline{A + B})$$

- (iii) Implement Boolean expression using only universal gates.

$$Y = ((\overline{A + B})C).D$$

- (iv) Interfacing CMOS and TTL Devices.

- (v) Convert Boolean function into standard SOP.

$$Y(A, B, C) = AB + A\overline{C} + BC \quad 15$$

- ~~5.~~ (a) Explain complex programmable logic devices. 5

- (b) Briefly explain the working of Dynamic RAM cell. Also explain MROM, PROM, EPROM, EEPROM. 10

6. (a) Implement the following function using 8:1 MUX : 10

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 7, 8, 9, 11, 14, 15)$$

- (b) Explain 4-bit buffer Register with suitable logic diagram. 5

- ~~7.~~ Explain 3-bit R-2R ladder *r* type DAC, converter with suitable diagram. And give its advantages and disadvantages and give specifications of DAC.

15