

**J C Bose University of Science and Technology, YMCA, Faridabad**  
**Subject: Analog Electronics Circuits (ESC-301)**  
**BTech 3<sup>rd</sup> Semester CE31**

Time: 90 minutes

M.M: 30



**Sessional Test I**  
**Oct, 2024**

Note: All questions are compulsory.



Q1. Draw the circuit diagram of centre tap full wave rectifier and explain its working. Also determine (i) average dc output current (ii) rms output current (iii) rms value of ac component of output waveform (iv) ripple factor (v) rectification efficiency (vi) PIV. (6) (CO1) (LOCQ)

Q2. The four diodes used in a bridge rectifier circuit have forward resistance of  $10\Omega$  and load resistance of  $480\Omega$ . The alternating supply voltage is 240V (rms). Calculate (i) average dc load current (ii) rms output current (iii) power loss in each diode (iv) rectification efficiency (v) ripple factor (vi) PIV. (6) (CO2) (LOCQ)

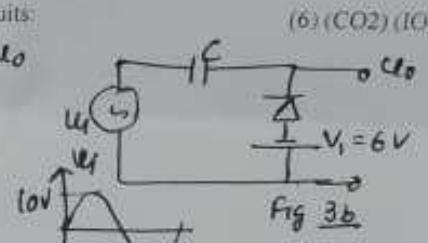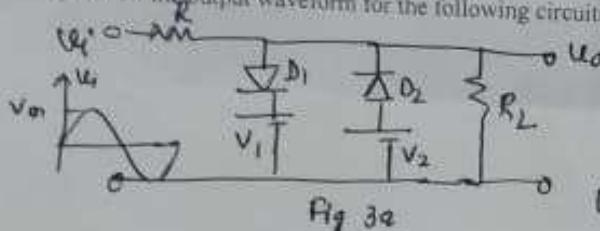Q3. Draw the output waveform for the following circuits. (6) (CO2) (LOCQ)



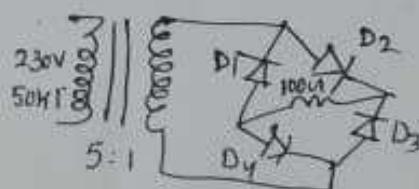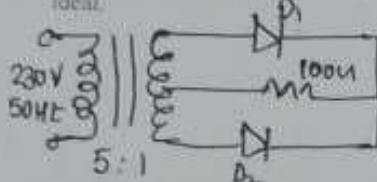Q4. For the given circuit find (i) dc output voltage in each case. (ii) PIV for each case. Assume diodes are ideal. (4) (CO2) (LOCQ)



Q5. (a) In a transistor operating in active region, although the collector junction is reverse biased, the collector current is quite large. Explain. (2) (CO2) (LOCQ)

(b) If the output voltage of a centre tap full wave rectifier and bridge rectifier is 50V. Determine the peak inverse voltage in both cases. (2) (CO2) (LOCQ)

(c) A full wave rectifier delivers 10W to a load of  $1000\Omega$ . If the ripple factor is 2%, calculate the ac ripple voltage across the load. (2) (CO2) (LOCQ)

(d) A power supply X delivers 10Vdc with a ripple of 0.5 volts rms, while the power supply Y delivers 25V dc with a ripple of 1mV rms. Which is better power supply and why? (2) (CO2) (LOCQ)

23001n2200

J.C.BOSE University of Science and Technology, YMCA Faridabad  
Subject: Analog Electronics Circuits (ESC-301)

BTech3rdSem CE32

Time: 90 minutes Sessional Test I

M.M: 30Oct, 2024


Note(i) All questions are compulsory.

Q1. Draw the circuit diagram of centre tap full wave rectifier and explain its working. Also determine (i) average dc output current (ii) rms output current (iii) ripple factor (iv) rectification efficiency (v) PIV. (5)

Q2. (a) Write down the characteristics of an ideal op amp (3)

(b) The differential voltage gain and CMRR of an op amp when expressed in decibels are 110 db and 100 db respectively. Calculate the common mode gain.(2)

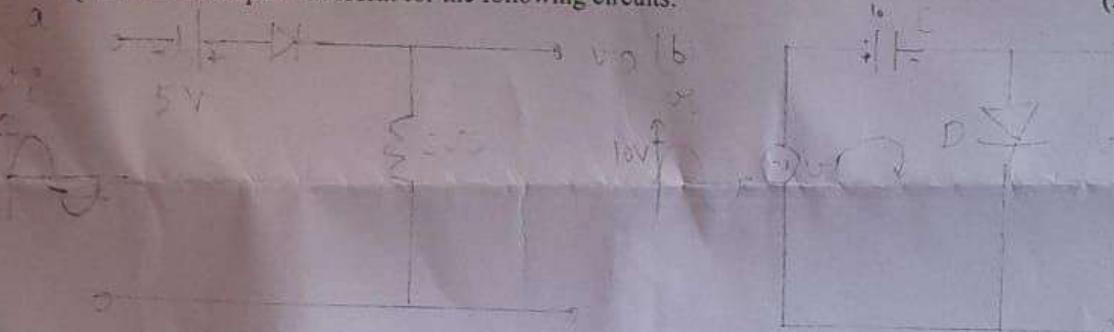Q3. Draw the output waveform for the following circuits: (5)



Q4. Draw the output characteristics of Common Emitter amplifier for a pnp transistor. Clearly indicate active, saturation and cut off region and also explain it. Also define  $\alpha$  and  $\beta$ , find the relation between them. (5)

Q5 (a) In a transistor operating in active region, although the collector junction is reversed biased, the collector current is quite large. Explain. (2)

(b) Determine the value of emitter current and collector current of a transistor having  $\alpha = 0.98$  and collector to base current  $I_{CBO} = 4\mu A$ . The base current is  $50\mu A$ . (3)

Q6. Explain the working of op amp as an inverting amplifier. (5)

930 v 3060

J C Bose University of Science and Technology, YMCA, Faridabad

Subject: Analog Electronics Circuits (ESC-301)

BTech 3<sup>rd</sup> Semester CE31

Time: 90 minutes

M.M: 30

Sessional Test II

Dec, 2024

Note: All questions are compulsory.

Q1. Derive the expression of current gain ( $A_i$ ), input impedance ( $Z_i$ ), voltage gain( $A_v$ ) and output impedance ( $Z_o$ ) in terms of  $b_i$ ,  $i_{sr}$ ,  $h_f$ ,  $h_o$ . (6) (CO2) (IOCQ)

Q2. A NPN transistor circuit uses the voltage divider method of biasing having  $\alpha = 0.985$  and  $V_{BE} = 0.3V$ . If  $V_{CC} = 15V$ , Calculate  $R_1$  and  $R_C$  to place Q point at  $I_C = 2mA$  and  $V_{CE} = 4V$ . The value of  $R_E = 2k\Omega$  and  $R_L = 20k\Omega$ . (6) (CO2) (HOCQ)

Q3. Draw the circuit diagram of RC Phase Shift Oscillator. Explain its working. Also derive the frequency of oscillations. (6) (CO3) (IOCQ)

Q4. Draw and explain the following circuit using opamp: (6)(CO4) (IOCQ)

- (i) Integrator
- (ii) Schmitt trigger

Q5. Find the expression of output voltage for the circuit given below. (6)(CO4) (HOCQ)

