

Roll No.

Total Pages : 3

008302

December 2023

B.Tech (ECE)- IIIrd SEMESTER

Digital System Design (EC-302)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) What is radix? Discuss with example. (1.5)
- (b) State the De-Morgan's theorem. (1.5)
- (c) Convert $(11101101)_2 = (\text{-----})_{\text{gray code}}$. (1.5)
- (d) Write the complete expression and logic circuit for the minterm designation $Y = \sum m(1,3,5,7)$.
- (e) Add two BCD numbers, $(0101) + (0110) = (-)_{\text{BCD}}$. (1.5)
- (f) What are the applications of Multiplexer (MUX)? (1.5)
- (g) What are the differences between latch and flip-flop circuits? (1.5)

008302/240/111/324

10 [P.T.O.]

- (h) What are the major differences between register and counter circuits? (1.5)
- (i) Define Fan-in and Fan-out? (1.5)
- (j) Define VHDL and its uses in digital system. (1.5)

PART-B

- 2. (a) Design a combinational circuit that generates the 9's complement of BCD inputs. (10)
- (b) Implement the following function using NAND gates only. (5)

$$F = A(B + CD) + BC'$$

- 3. (a) Implement a full adder circuit with 3×8 decoder and two OR gates. (5)
- (b) Simplify the following expression using K-map. (10)

$$F(A, B, C, D, E) = \sum m(0, 2, 5, 7, 8, 10, 16, 21, 23, 24, 27, 31).$$

- 4. Design a synchronous counter for count the sequence 4, 6, 7, 3, 1, 4... avoid lockout condition and use JK flip-flop. (15)

- 5. (a) What is the race around condition? And how it can be eliminated, discuss through diagram? (5)
- (b) Convert the SR to JK flip-flop with the circuit diagram and verify the final circuit through justification. (10)

- 6. (a) Compare ECL and TTL families on Noise margin, Propagation delay, fan-in, fan-out with minimum 10 points. (10)
- (b) Draw TTL with Totem-Pole configuration and explain its working in details. (5)
- 7. Explain Data types and objects, Dataflow, Behavioural and Structural Modelling, Synthesis in VHDL. Write a program for half adder execution in VHDL. (15)