

Roll No. ....23001008063

Total Pages : 06

**008303**

**December 2024**

**B. Tech. (ECE) (Third Semester)**

**Network Theory (EC-304)**

*Time : 3 Hours]*

*[Maximum Marks : 75]*

**Note :** It is compulsory to answer all the questions (1.5 marks each) of Part A in short. Answer any *four* questions from Part B in detail. Different sub-parts of a question are to be attempted adjacent to each other.

**Part A**

1. (a) Synthesize the following wave in terms of standard signals. **1.5**

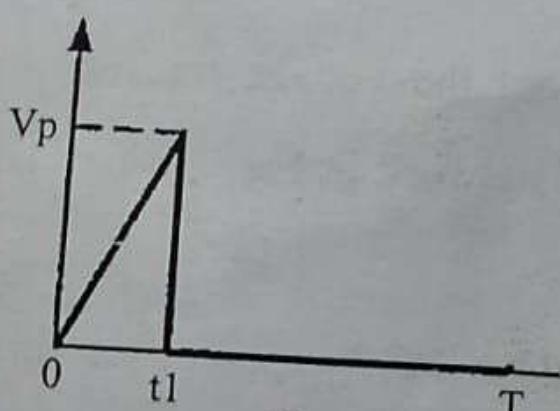


Fig. 1

(b) In a series combination of  $R$  and  $L$ , the inductor is having initial current of 1 A. Derive an expression for current through inductor for time  $t > 0$ . 1.5

(c) Find the Laplace transform of  $M * (t-a) * u(t)$ . 1.5

(d) Find out the transfer admittance  $Y_{21}(s)$  of the following network where  $R_1=R_2=R_3=1$  ohm. 1.5

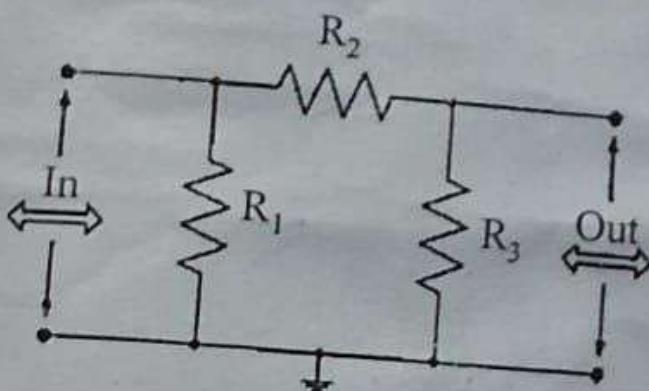


Fig. 2

(e) Find out the voltage transfer ratio  $V_{21}(s)$  of the network in Fig. 2 where  $R_1=R_2=R_3=1$  ohm. 1.5

(f) Calculate the  $Z_{11}$  parameter for network in Fig. 2. 1.5

- (g) State with reasons whether the following function suitable as current transfer function or not ? 1.5

$$F(s) = \frac{s^2 + 1}{s^2(s + 2)}$$

- (h) Calculate the value of characteristics impedance,  $Z$  of T section of high pass filter having  $R_0 = 500$  Ohm,  $f = 1000$  Hz,  $f_c = 800$  Hz. 1.5
- (i) Calculate Fourier Transform  $F(w)$  for waveform in Fig. 3. 1.5


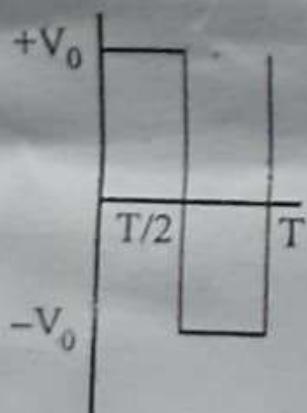


Fig. 3

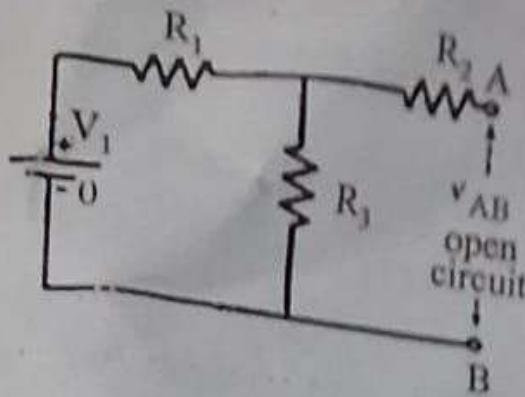- (j) Find the Norton current for the following circuit between point AB with  $R_1 = R_2 = R_3 = 1$  ohm and  $V_1 = 10$  V. 1.5




### Part B


2. (a) Find Laplace transform of  $\exp(-at) * \cosh(bt) * u(t)$ . 7.5

- (b) Obtain the value of current  $i(t)$  in the circuit given below to  $v(t) = 20 \sin(1000t + 45^\circ)$  for  $R = 1 \text{ ohm}$ ,  $L = 1 \text{ mH}$ . 7.5


20/45

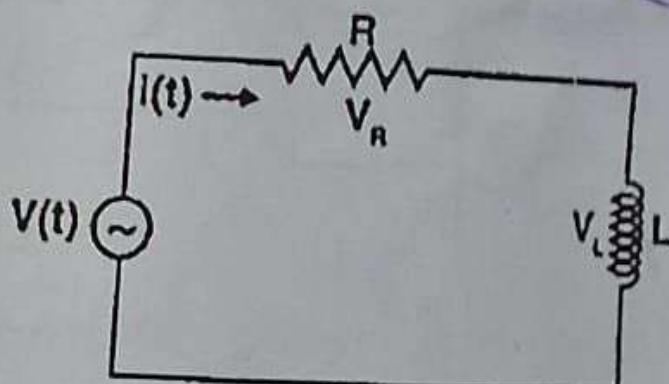

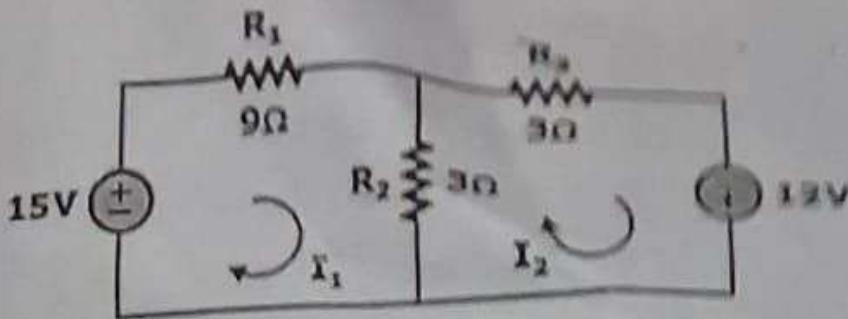
3. (a) Verify the Tellegen Theorem for the following network : 7.5



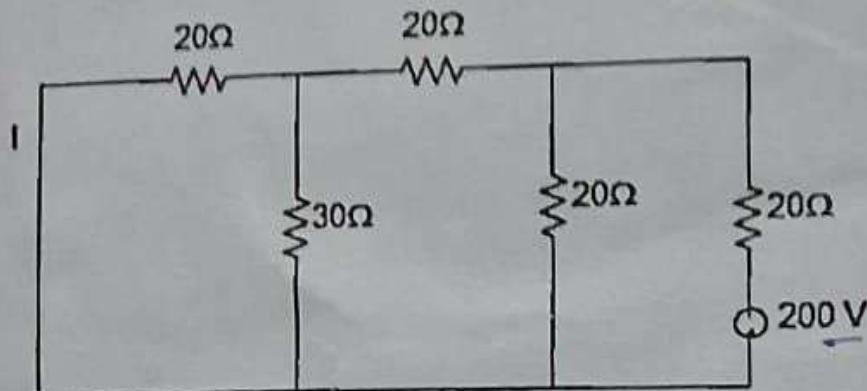
- (b) Solve for currents in all the branches using  
nodal analysis. 7.5



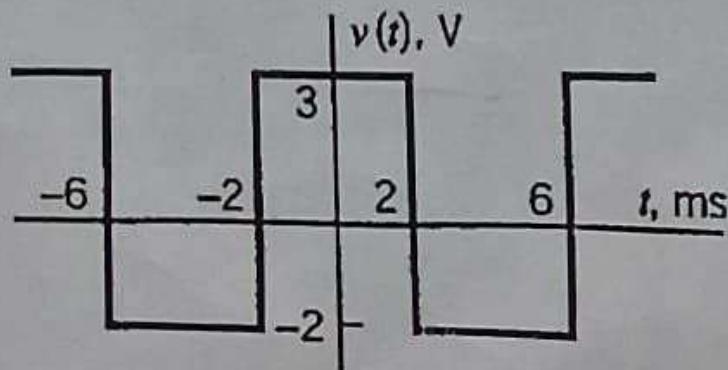4. (a) Calculate Fourier transform of waveform in Fig. 3. 7.5
- (b) Find Fourier series of the following waveforms. 7.5



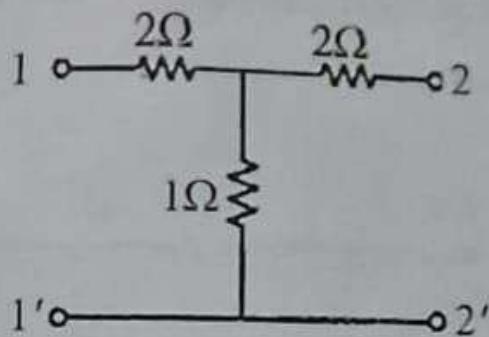5. (a) Express  $Z$  parameter in terms of  $Y$  parameters. 7.5  
 ✓ (b) State necessary condition for driving point function. 7.5
6. (a) Find the voltage transfer function  $V_2(s)/V_1(s)$  with output open circuited. 7.5  
 ✓



- (b) Design low pass filter with  $R_0 = 600$  ohm,  $f_c = 600$  Hz. 7.5
7. (a) Design a high pass filter with  $F_0 = 600$  ohm,  $f_c = 600$  Hz. 7.5  
 (b) Find convolution of two pulses. 7.5

