

Roll No. ....

Total Pages : 6

**008303**

**December 2023**

**B.Tech. (ECE) IIIrd SEMESTER**

**Network Theory (EC-304)**

Time : 3 Hours]

[Max. Marks : 75

*Instructions :*

1. It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.
2. Answer any four questions from Part-B in detail.
3. Different sub-parts of a question are to be attempted adjacent to each other.

**PART-A**

1. (a) Synthesize the following half cycle of sine wave in terms of standard signals (CO5) (1.5)

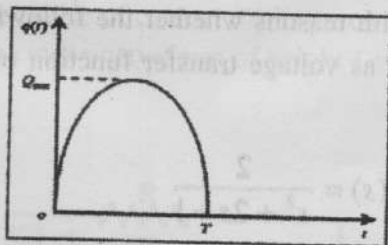


Figure 1

- (b) In a parallel combination of R and C, the capacitor is initially charged to a voltage V. Derive an expression for voltage across this capacitor for time  $t > 0$ .

(CO1) (1.5)

- (c) Find the Laplace transform of  $\cosh(at) * u(t)$ . (CO3) (1.5)

- (d) Find out the transfer impedance  $Z_{21}(s)$  of the following network. (CO4) (1.5)

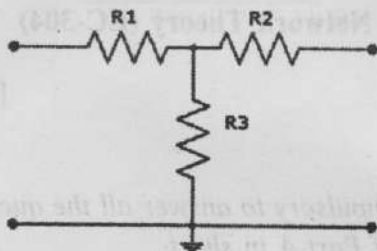


Figure 2

- (e) Find out the voltage transfer ratio  $V_{21}(s)$  of the network in Figure 2. (CO4) (1.5)

- (f) Calculate the B parameter for network in Figure 2. (CO4) (1.5)


- (g) State with reasons whether the following functions are suitable as voltage transfer function or not? (CO4) (1.5)

(i)  $H(s) = \frac{2}{s^2 + 2s + 1}$

(ii)  $H(s) = \frac{2s^2}{s^2 + 2s + 1}$


(iii)  $H(s) = \frac{s}{s^2 + 0.2s + 100}$

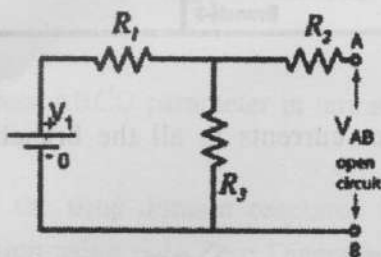- (h) Calculate the value of characteristics impedance,  $Z$  of T section of low pass filter having  $R_0 = 600 \text{ Ohm}$ ,  $f = 600 \text{ Hz}$ ,  $f_c = 1000 \text{ Hz}$ . (CO5) (1.5)
- (i) Calculate inverse Fourier Transform  $f(t)$  of  $\delta(w)$ . (CO5) (1.5)
- (j) Find the Thevenin voltage for following circuit between point AB with  $R_1 = R_2 = R_3 = 1 \text{ ohm}$ . (CO2) (1.5)




### PART-B

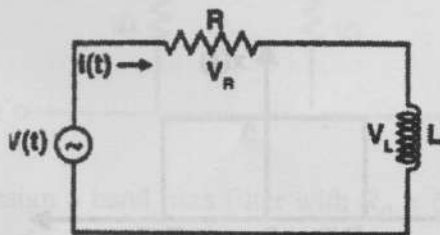
2. (a) State and prove maximum power transfer theorem for AC circuit. (CO2) (7.5)
- (b) Obtain the value of current  $i(t)$  in the circuit given below to  $v(t)$ , the pulse waveform of height 1 volt and duration 1 sec. (CO2) (7.5)



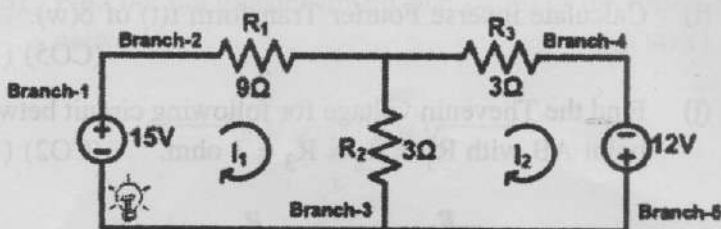
3. (a) Verify the Tellegen Theorem for the following network:  
(CO2) (7.5)



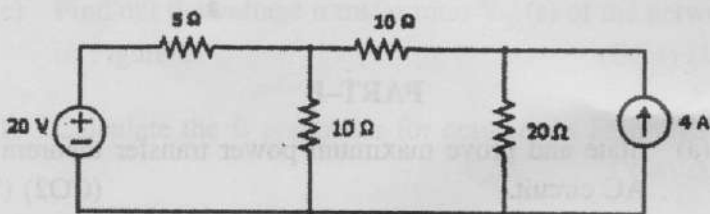- (b) Solve for currents in all the branches using nodal analysis.  
(CO1) (7.5)




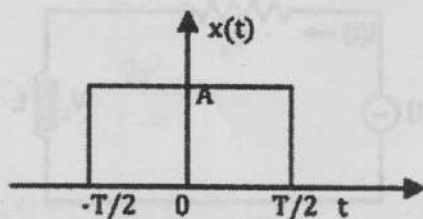4. (a) Calculate Fourier transform of following waveform  
(CO5) (7.5)



- (b) Find Fourier series of following waveforms.

(CO5) (7.5)

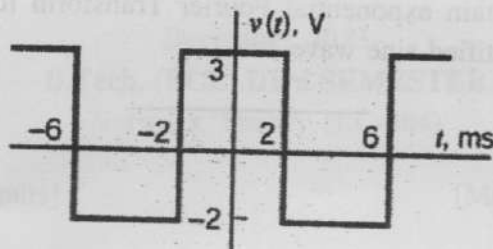

5. (a) Express ABCD parameter in terms of Z parameters.

(CO4) (7.5)


- (b) Find the time domain response  $f(t)$  from following function using pole Zero Diagram.

(CO3) (7.5)

$$F(s) = 10 \cdot \frac{(s+1)(s+2)}{(s+4)(s+5)(s+8)}$$

6. (a) Find the voltage transfer function  $V_2(s)/V_1(s)$  with output open circuited.

(CO4) (7.5)

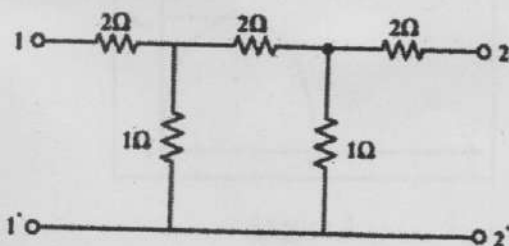

- (b) Design a band pass filter with  $R_0 = 600 \text{ ohm}$ ,  $f_1 = 600 \text{ Hz}$ ,  $f_2 = 1200 \text{ Hz}$ .

(CO5) (7.5)

7. (a) For a T type filter, derive condition for pass band. (CO5) (7.5)
- (b) Obtain exponential Fourier Transform for half wave rectified sine wave. (CO3) (7.5)