

January 2023

B.Tech- III SEMESTER

Circuit Analysis and Synthesis (ECP 305)

Time: 3 Hours

Max. Marks:75

Instructions:


1. It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.
2. Answer any four questions from Part -B in detail.
3. Different sub-parts of a question are to be attempted adjacent to each other.

PART -A

- Q1 (a) State compensation theorem. When is the use of this theorem preferred in solution of ac networks? (1.5)
- (b) In what respects are Kirchoff's laws as applicable to ac circuits different from those for dc circuits? (1.5)
- (c) How is the concept of transfer function important in system studies? (1.5)
- (d) Determine the initial value $f(0^+)$, if $F(s) = \frac{2(s+1)}{s^2+2s+5}$ (1.5)
- (e) Draw the equivalent circuit of a two port network in terms of Z-parameters. (1.5)
- (f) Derive the condition for reciprocity in case of T-parameters. (1.5)
- (g) List the network functions of a two port network. (1.5)
- (h) Obtain the pole zero plot of the following function $f(t) = \cos \omega t$. (1.5)
- (i) What are the units of attenuation? (1.5)
- (j) Define all the parameters of a filter. (1.5)


PART -B

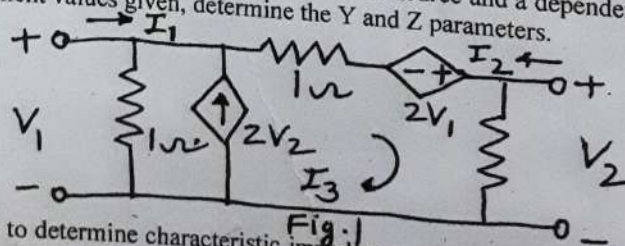- Q2 (a) Obtain the h-parameters of the network in terms of all other parameters. (7.5)
- (b) The network of Fig. 1 contains both a dependent current source and a dependent voltage source. For the element values given, determine the Y and Z parameters. (7.5)




- Q3 Derive expressions to determine characteristic impedance, cut off frequency, attenuation and phase constant of a constant- K high pass filter and also draw variation of all characteristics with frequency. Design a high pass filter (both π and T-networks) having a cut off frequency of 2 kHz to operate with a terminated load resistance of 300 Ω . (15)
- Q4 (a) Discuss the graphical procedure to determine time domain response from the pole zero plot with a suitable example. (7.5)

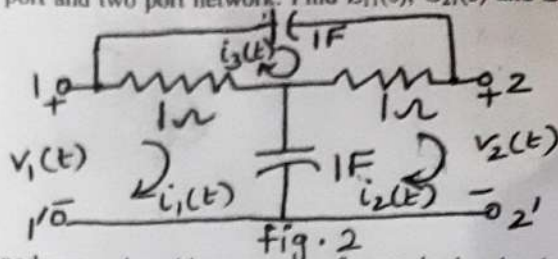
- (b) Differentiate between one port and two port network. Find $Z_{11}(s)$, $G_{21}(s)$ and $Z_{21}(s)$ for (7.5) the circuit of Fig.2



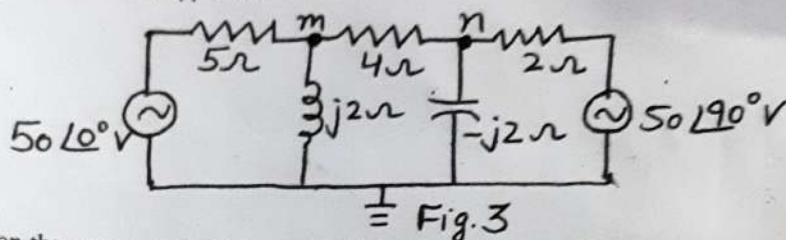
- Q5 (a) Determine the voltages of nodes m and n with respect to reference in the circuit of Fig.3 (7.5) using nodal analysis. Use matrix approach.



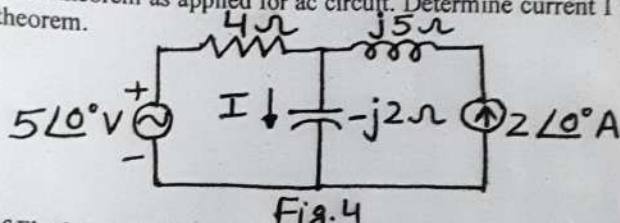- (b) State superposition theorem as applied for ac circuit. Determine current I in Fig.4, using (7.5) superposition theorem.




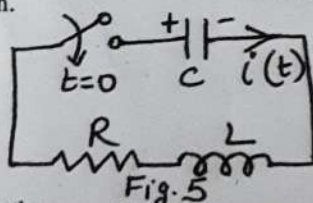- Q6 (a) In the circuit of Fig.5, $L = 2H$, $R = 12\Omega$ and $C = 62.5mF$. The initial conditions are $v_c(0+) = 100V$ and $i_L(0+) = 1.0A$. The switch is closed at $t=0$. Find $i(t)$ using Laplace transform and partial fraction expansion.



- (b) State and prove time shifting theorem of Laplace transform. Find the Laplace transform (7.5) of the following function: $f(t) = e^{-at} \sin \omega t$.

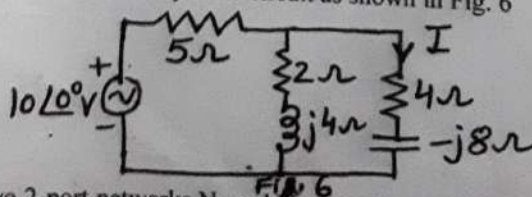- Q7 (a) State reciprocity theorem and verify it for circuit as shown in Fig. 6



- (b) Show that when two 2-port networks N_1 and N_2 are connected in parallel, the equivalent (7.5) Y-parameters of the combined network is the sum of Y-parameters of each individual 2-port network.
