

Roll No. ....23001017055

Total Pages : 07

**017304**

**December 2024**

**B.Tech. (EE/ENC) (Third Semester)**

**Circuit Analysis and Synthesis (ECP305)**

*Time : 3 Hours]*

*[Maximum Marks : 75]*

**Note :** It is compulsory to answer all the questions

(1.5 marks each) of Part A in short. Answer

any *four* questions from Part B in detail.

Different sub-parts of a question are to be

attempted adjacent to each other.

### **Part A**

1. (a)  Determine h-parameters if the Y-parameters

are :  $Y_{11} = 0.1 \text{ mho}$ ;  $Y_{21} = 0.4 \text{ mho}$ ;

$Y_{12} = 0.1 \text{ mho}$ ;  $Y_{22} = 0.5 \text{ mho}$ . **1.5**

(b)  Define transfer function of a circuit. **1.5**

- (c) Why should low pass filters have inductance in series arm and capacitance in shunt arm ? **1.5**
- (d) Find initial value and final value for the function  $F(s) = \frac{10(s+2)}{(s+1)(s+3)}$  **1.5**
- (e) Derive the condition for reciprocity for Y-parameter. **1.5**
- (f) Define all the characteristics of filter networks. **1.5**
- (g) What is the significance of poles and zeros of network functions ? **1.5**
- (h) Find the Laplace transform of  $f(t) = \cos\omega t$ . **1.5**
- (i) Why are Z - parameters called open circuit impedance parameters ? **1.5**
- (j) What is the value of load impedance if internal impedance is  $5-j5\Omega$  for maximum power transfer in A.C circuit ? **1.5**

### Part B

2. (a) Show that when two 2 -port networks  $N_1$  and  $N_2$  are connected in parallel, the equivalent Y-parameters of the combined network is the sum of Y-parameters of each individual 2 -port network. **7.5**
- (b) Determine the Z-parameters and ABCD parameters of the circuit shown in Fig.1. **7.5**

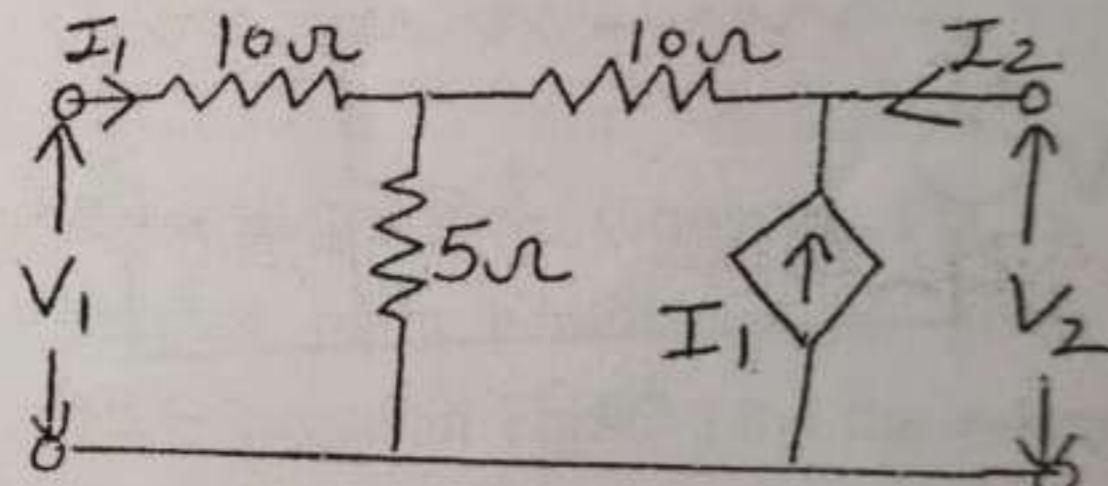


Fig. (1)

3. (a) In what respect high pass filter is different than low pass filter. Derive expressions to determine cut off frequency, inductance and capacitance of high pass filter. **7.5**

(b) Design a band pass filter having a pass band from 500Hz to 5000Hz and a characteristic resistance of 100 ohms. 7.5

4. Draw the dual of a given network in Fig.2. In the network shown in Fig. 3, find  $V_o$  using nodal method. Use matrix approach for analysis. 15

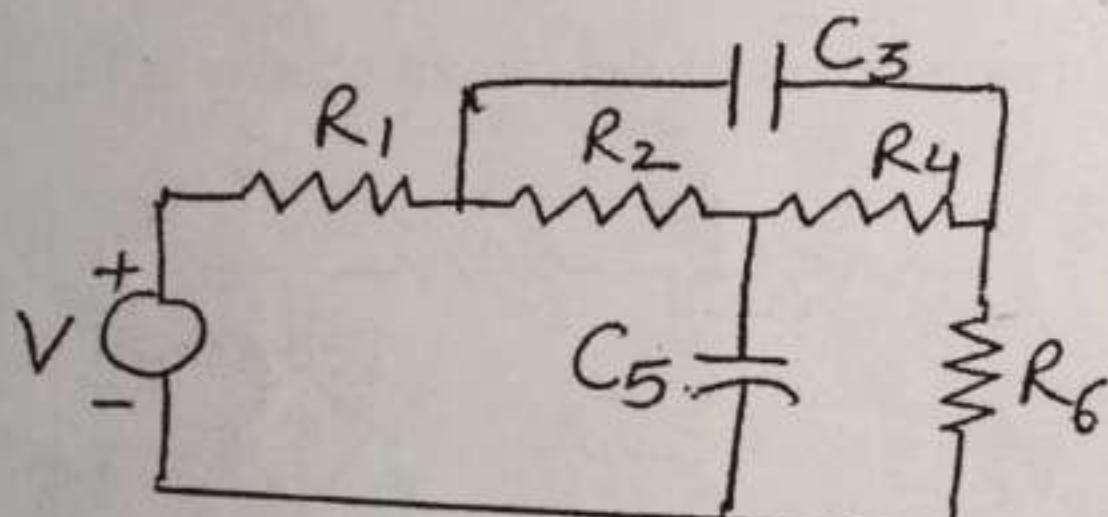


Fig. 2

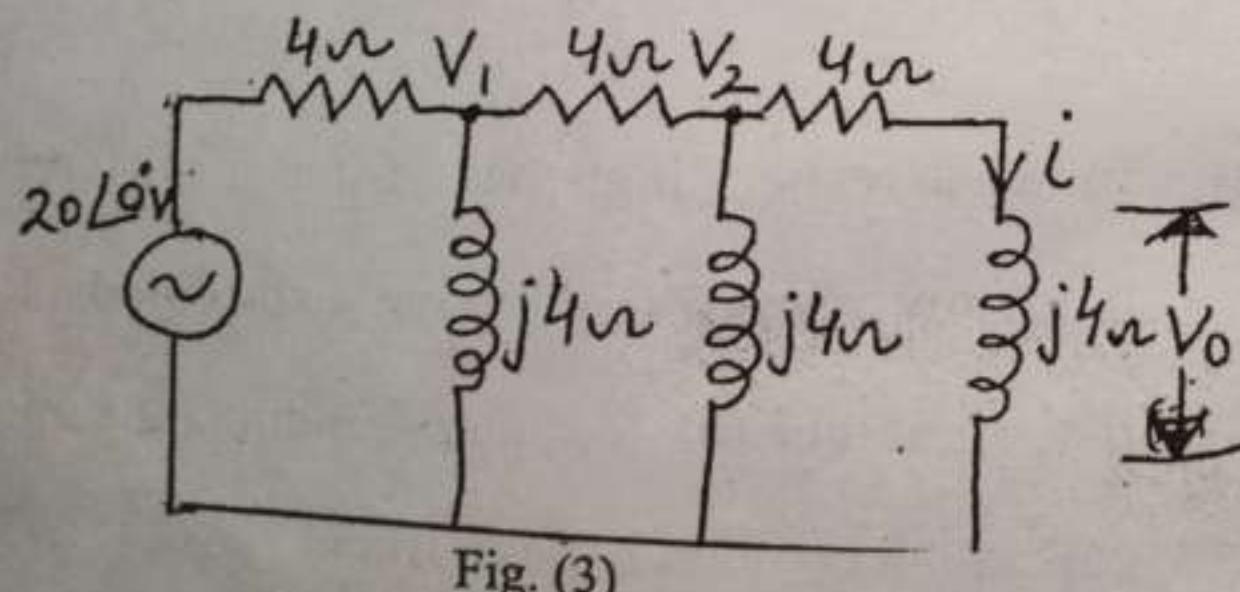


Fig. (3)

C-017304

4

5. (a) Write the necessary conditions for driving point functions. Find the following network functions :

$$\frac{V_2(s)}{V_1(s)}, \frac{V_2(s)}{I_1(s)} \text{ and } \frac{V_1(s)}{I_1(s)}$$

for the circuit shown in Fig.4.

10

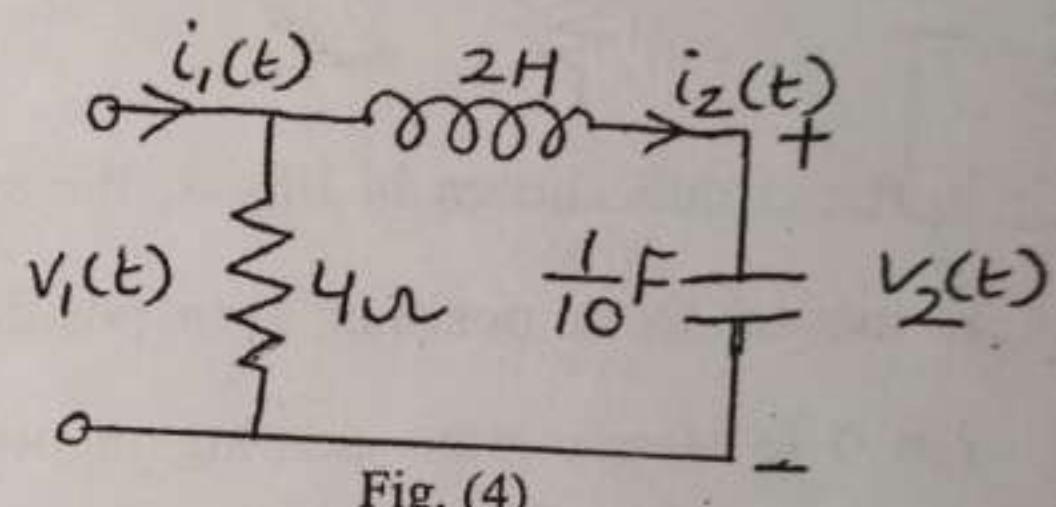


Fig. (4)

(b) A network function obtained using a pole 'zero' diagram as shown in Fig. 5, is the driving point admittance for given series RLC circuit in Fig. 6. Find the values of R, L and C. 5

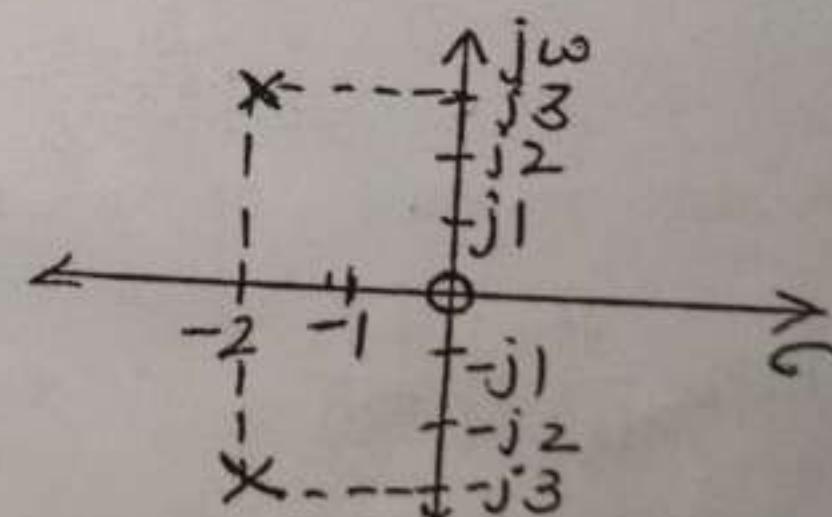


Fig. (5)

3-M24-08/5) C-017304

5

P.T.O.

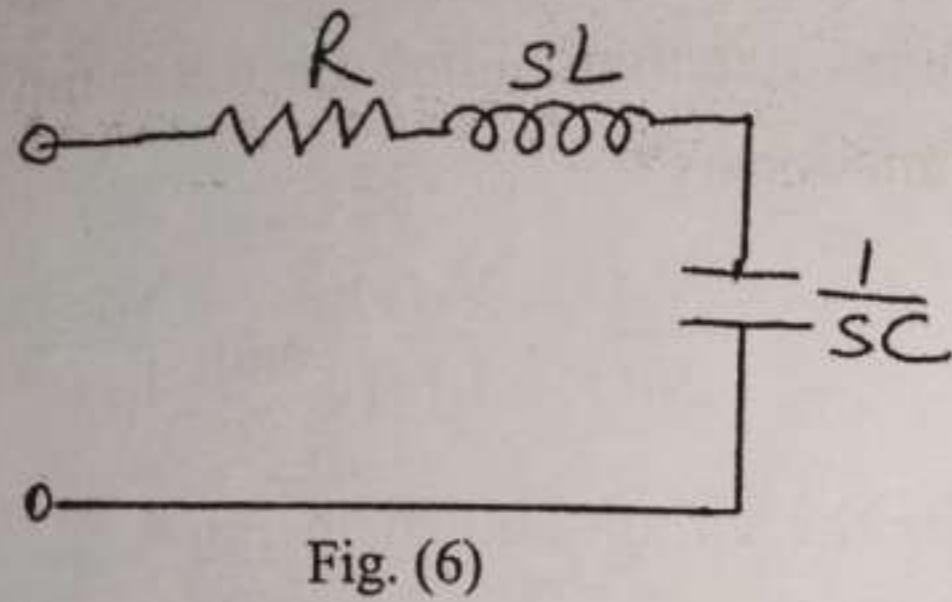


Fig. (6)

6. (a) In the circuit shown in Fig. 7, the switch S is moved from position 1 to position 2 at  $t = 0$  (a steady state existing in position 1 before  $t = 0$ ). Solve for the current  $i_L(t)$ . 7.5

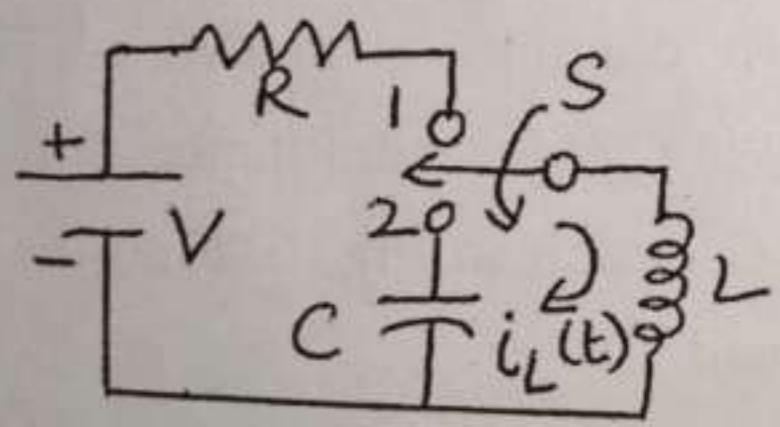


Fig. (7)

- (b) Find the response of a network

$$\text{if } H(s) = \frac{s^2 + 3s + 5}{(s+1)(s+2)} \quad \text{and excitation}$$

$$x(t) = e^{-3t} u(t).$$

14

- ✓ 7. Discuss Tellegen's and Reciprocity theorem. Find current I through  $2\Omega$  resistance using Thevenin's theorem for the given circuit in Fig.8. 15

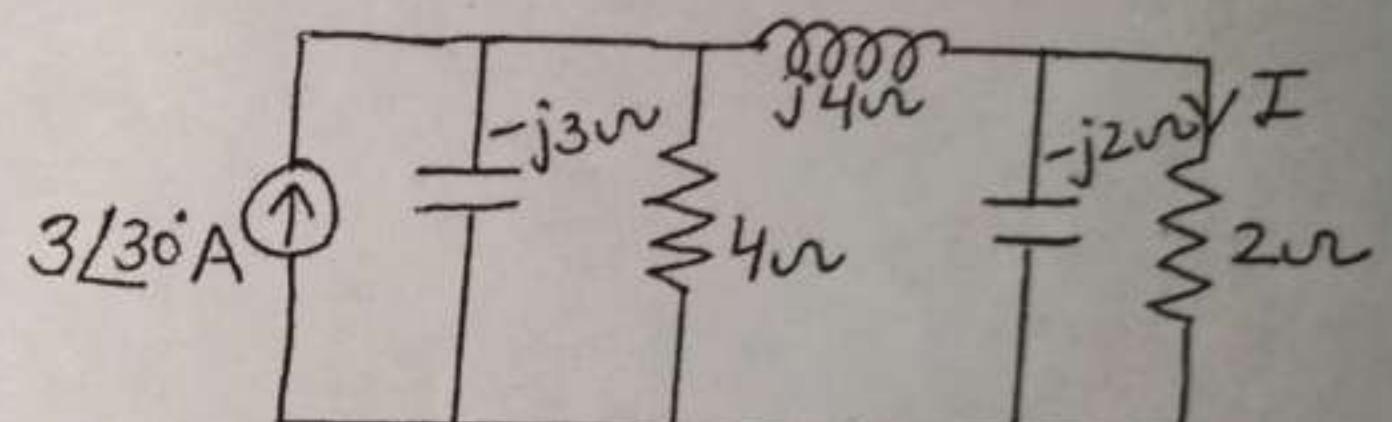


Fig. (8)