

①

Roll No.

Total Pages : 3

017301

Mar. 2022

B.Tech. (EIOT) - III SEMESTER

Digital Electronics (EEN-301)

Time : 90 Minutes]

[Max. Marks : 25

Instructions :

1. *It is compulsory to answer all the questions (1 mark each) of Part-A in short.*
2. *Answer any three questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) Implement the NOR gate using the NAND gate only. (1)
- (b) What is a demultiplexer? (1)
- (c) Convert $(111.10)_2$ into equivalent Hexadecimal code. (1)
- (d) Find $(125)_8 / (25)_{10} = (\dots)_{10}$. (1)
- (e) Differentiate between 'T' and 'D' Flip-flop. (1)
- (f) What are asynchronous counters? (1)

- (g) What do you mean by quantization for A/D converters? (1)
- (h) What is the purpose of using PLD? (1)
- (i) Write the truth table of Full adder. (1)
- (j) How Ring counter is different from Johnson counter? (1)

PART-B

2. Minimize the following function using Quine Mcclusky method
 $f(A, B, C, D) = \sum m(0, 2, 5, 11, 13) + \sum d(1, 6, 14)$. (5)
3. (a) What is the error detection and correction codes? How these are helpful in error detection and correction explain with the help of an example. (3)
- (b) Differentiate between serial carry and carry look-ahead adders with suitable diagrams. (2)
4. Design a Mod-10 counter using flip-flops. (5)
5. (a) Perform the following :
- (i) $(12.5)_{10} \rightarrow ()_{16}$.
- (ii) $(87.16)_8 \rightarrow ()_2$.
- (iii) $(101110)_2 \rightarrow ()_{\text{Gray code}}$. (3)

- (b) Implement half adder using 4:1 multiplexer. (2)
6. (a) Define resolution, sensitivity and accuracy of A/D converter. (3)
- (b) Differentiate between PLA and PAL. (2)